

Learning Experience C.3 Project Report
ECE 2544

Objective and Requirements

The objective of Learning Experience C was to create two key components of a simple computer: an 8-bit function unit and a register transfer system, where the function unit is capable of implementing 13 distinct operations on two 8-bit operands as well as outputting four status bits, and there are four 8-bit registers capable of storing data from switches, storing data from the function unit, and sending data to the function unit. The function unit had to accept a four bit function select code to choose the operation, each operation had to have a unique code, the entire circuit had to be designed and simulated in Quartus Prime Lite Edition using structural and/or dataflow Verilog, and the circuit had to be designed to minimize FPGA resource usage. In addition to designing the circuit, part 3 of Learning Experience C, also referred to throughout this document as LE C.3, required the creation of a network diagram for the main deliverables of the assignment. This network diagram can be found in Diagram 1, where the main deliverables are colored in yellow.

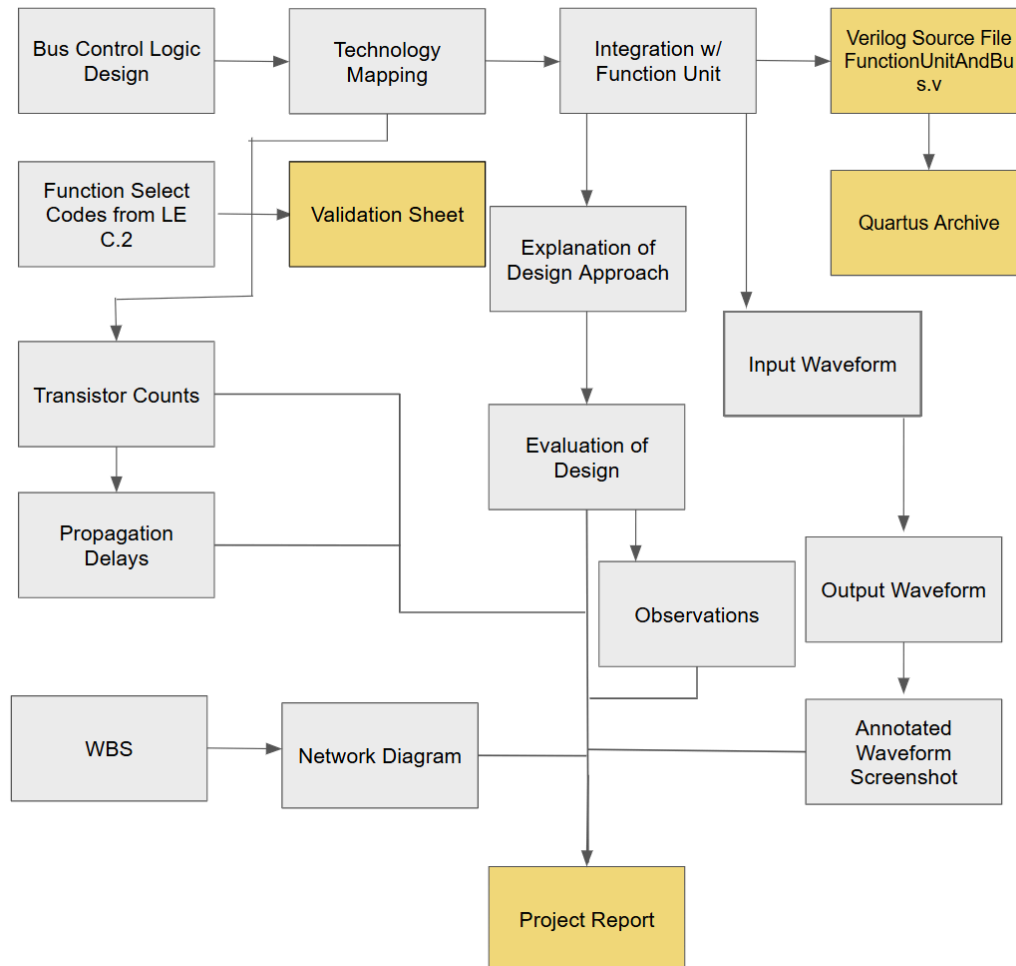


Diagram 1: Learning Experience C.3 Network Diagram

Circuit Design

The same function unit from LE C.2 was used in this learning experience. The function unit was designed with a combination of ripple carry adders, muxes, decoders, and XOR gates. The function unit's 13 operations were divided into three separate units, involving an arithmetic unit, a logic unit, and a shifting unit. Given the operands and the function select code, each functional block computed an 8-bit output, though only one of the functional blocks produced an output corresponding to the actual operation. Each bit of the three outputs was sent to a 3 x 1 mux along with the first three bits of the function select code to choose which bit would be passed through to the final output. Three bits were used instead of two since both the arithmetic block and logic block contained more than 4 operations. If only two bits from the function select code were preserved to indicate the proper functional block, then each operation would only be distinguished by the remaining two bits, which would only allow each block to contain four operations. By using three bits, the part of the function select code that corresponded to the functional block could overlap with the remaining code, allowing for 13 unique operation codes and the ability to select between 3 distinct functional blocks. To simplify the control logic, codes corresponding to the arithmetic operations ended in a 1 if the carry-in bit of the operation needed to be a 1, otherwise they ended in a 0. To produce the status bits, the N bit was set to equal the most significant bit of the output, the Z bit was equivalent to putting every output bit through one large NOR gate, and the arithmetic block was modified to output the carry out and carry in bits of the most significant bit to get the values for V and C. C was set equal to the value of the carry out bit, and a XOR gate was used between the carry out and carry in bit to get the value of V. The register transfer system was designed such that a 2 x 4 decoder was used to control the load signal for each register, using input switches SW[1] and SW[0] to determine which register would receive the load signal. Each bit of each register was sent to a 4 x 1 mux along with the corresponding switch values to determine which register's value would get sent to the operandA bus, and a second set of muxes was used in the same way to determine which register's value would get sent to the operandB bus. The two buses were used as inputs to the function unit. The function unit then sent its output to a 2 x 1 mux along with the switch values SW[9:2], and which one was sent to the registers to be loaded in was based on which button was being pressed. All circuits and functional units were technology mapped wherever possible to minimize transistor usage, replacing most AND/OR logic with NAND gates. Circuits that relied primarily on AND gates and inverters, such as most of the decoders, were not technology mapped since there would have been no reduction in transistor usage. The transistor counts for the function unit and its functional blocks can be found in Tables 1.1 - 1.10, the transistor counts for the register transfer system can be found in Tables 1.11 - 1.17, and the total transistor count for LE C.3 can be found in Table 1.18. Note that the 8-bit 2x1 mux for the circuit was assumed to be implemented using just AND and OR gates, since no inverters were seen in its implementation in the Verilog code. The propagation delays for the critical path of the different functional blocks and the function unit can be found in Tables 2.1 - 2.5, the propagation delays for the critical path of the register transfer system can be found in Tables 2.6 - 2.9, and the propagation delay for the critical path of the whole circuit can be found in Table 2.10. Due to the looping nature of the circuit, the critical path for this circuit was defined as the path from an input

control signal to the 2x4 loading decoder of the register transfer system all the way to the output of the function unit.

| Gate Type | Transistors in Gate | Number of Gates | Total Transistors |
|-------------|---------------------|-----------------|-------------------|
| inverter | 2 | 4 | 8 |
| 4-input AND | 10 | 5 | 50 |
| 4-input NOR | 8 | 1 | 8 |
| | | | 66 |

Table 1.1: Transistors for the 4x6 decoder for the arithmetic functional block

| Gate Type | Transistors in Gate | Number of Gates | Total Transistors |
|-------------|---------------------|-----------------|-------------------|
| inverter | 2 | 4 | 8 |
| 4-input AND | 10 | 5 | 50 |
| | | | 58 |

Table 1.2: Transistors for the 4x5 decoder for the logic functional block

| Gate Type | Transistors in Gate | Number of Gates | Total Transistors |
|-------------|---------------------|-----------------|-------------------|
| inverter | 2 | 2 | 4 |
| 4-input AND | 10 | 2 | 20 |
| | | | 24 |

Table 1.3: Transistors for the 4x2 decoder for the shifting functional block

| Gate Type | Transistors in Gate | Number of Gates | Total Transistors |
|--------------|---------------------|-----------------|-------------------|
| inverter | 2 | 3 | 6 |
| 2-input NAND | 4 | 3 | 12 |
| 3-input NAND | 6 | 5 | 30 |
| 4-input NAND | 8 | 1 | 8 |
| | | | 56 |

Table 1.4: Transistors for the full adder

| Functional Block | Transistors in FB | Number of FBs | Total Transistors |
|------------------|-------------------|---------------|-------------------|
| Full Adder | 56 | 8 | 448 |
| | | | 448 |

Table 1.5: Transistors for the ripple carry adder

| Functional Block | Transistors in FB | Number of FBs | Total Transistors |
|--------------------|-------------------|---------------|-------------------|
| 4 x 6 Decoder | 66 | 1 | 66 |
| 3 x 1 Mux | 38 | 15 | 570 |
| 4 x 1 Mux | 38 | 1 | 38 |
| Ripple Carry Adder | 448 | 1 | 448 |
| | | | 1122 |

Table 1.6: Transistors for the arithmetic functional block

| Functional Block | Transistors in FB | Number of FBs | Total Transistors |
|--------------------|-------------------|---------------|-------------------|
| 5 x 1 mux | 30 | 8 | 240 |
| 5 x 1 mux's inputs | 16 | 8 | 128 |
| 4 x 5 decoder | 58 | 1 | 58 |
| | | | 426 |

Table 1.7: Transistors for the logical functional block

| Functional Block | Transistors in FB | Number of FBs | Total Transistors |
|--------------------|-------------------|---------------|-------------------|
| 4 x 2 decoder | 24 | 1 | 24 |
| 2 x 1 mux | 12 | 8 | 96 |
| Ripple Carry Adder | 448 | 1 | 448 |
| XOR gates | 96 | 1 | 96 |
| | | | 664 |

Table 1.8: Transistors for the shifting functional block

| Gate Type | Transistors in Gate | Number of Gates | Total Transistors |
|--------------|---------------------|-----------------|-------------------|
| 2-input NAND | 4 | 3 | 12 |
| 3-input NAND | 6 | 1 | 6 |
| | | | 18 |

Table 1.9: Transistors for the 3x1 mux for the function unit

| Gate/Block Type | Transistors in Gate | Number of Gates | Total Transistors |
|-----------------|---------------------|-----------------|-------------------|
| 8-input NOR | 16 | 1 | 16 |
| 2-input XOR | 12 | 1 | 12 |
| 3 x 1 mux | 18 | 2 | 36 |
| | | | 64 |

Table 1.10: Transistors for the status bit logic for the function unit

| Gate Type | Transistors in Gate | Number of Gates | Total Transistors |
|--------------|---------------------|-----------------|-------------------|
| inverter | 2 | 3 | 6 |
| 2-input NAND | 4 | 4 | 16 |
| 3-input NAND | 6 | 2 | 12 |
| 2-input AND | 6 | 1 | 6 |
| | | | 40 |

Table 1.11: Transistors for the 3x3 decoder for the function unit

| Gate / Block Type | Transistors in Gate/Block | Number of Gates/Blocks | Total Transistors |
|-------------------|---------------------------|------------------------|-------------------|
| Arithmetic FB | 1122 | 1 | 1122 |
| Logical FB | 426 | 1 | 426 |
| Shifting FB | 664 | 1 | 664 |
| 3 x 1 mux | 18 | 8 | 144 |
| 3 x 3 decoder | 40 | 1 | 40 |
| Status Bit Logic | 64 | 1 | 64 |
| | | | 2460 |

Table 1.12: Transistors for the function unit

| Gate Type | Transistors in Gate | Number of Gates | Total Transistors |
|-------------|---------------------|-----------------|-------------------|
| 2-input AND | 6 | 16 | 96 |
| 2-input OR | 6 | 8 | 48 |
| | | | 144 |

Table 1.13: Transistors for the 8-bit 2x1 mux for the register transfer system

| Gate Type | Transistors in Gate | Number of Gates | Total Transistors |
|--------------|---------------------|-----------------|-------------------|
| inverter | 2 | 2 | 4 |
| 2-input OR | 6 | 1 | 6 |
| 3-input NAND | 6 | 4 | 24 |
| | | | 34 |

Table 1.14: Transistors for the 2x4 decoder for the load signal of the register transfer system

| Gate Type | Transistors in Gate | Number of Gates | Total Transistors |
|--------------|---------------------|-----------------|-------------------|
| inverter | 2 | 2 | 4 |
| 2-input NAND | 4 | 4 | 16 |
| | | | 20 |

Table 1.15: Transistors for the 2x4 decoder for the 4x1 mux of the register transfer system

| Gate/Block Type | Transistors in Gate/Block | Number of Gates/Blocks | Total Transistors |
|-----------------|---------------------------|------------------------|-------------------|
| 2-input NAND | 4 | 4 | 16 |
| 4-input NAND | 8 | 1 | 8 |
| 2x4 Decoder | 20 | 1 | 20 |
| | | | 44 |

Table 1.16: Transistors for the 4x1 mux for the register transfer system

| Gate / Block Type | Transistors in Gate/Block | Number of Gates/Blocks | Total Transistors |
|-------------------|---------------------------|------------------------|-------------------|
| 8-bit 2x1 mux | 144 | 1 | 144 |
| 2x4 Load Decoder | 34 | 1 | 34 |
| 4x1 mux | 44 | 16 | 704 |
| | | | 882 |

Table 1.17: Total transistor count for the register transfer system

| Block/Circuit Type | Transistors in Block | Number of Blocks | Total Transistors |
|--------------------------|----------------------|------------------|-------------------|
| Register Transfer System | 882 | 1 | 882 |
| Function Unit | 2460 | 1 | 2460 |
| | | | 3342 |

Table 1.18: Total transistor count for the LE C.3 circuit

| Gate Type | Propagation Delay (ps) | Number of Gates in Critical Path | Total Propagation Delay (ps) |
|-------------|------------------------|----------------------------------|------------------------------|
| inverter | 25 | 1 | 25 |
| 4-input AND | 125 | 1 | 125 |
| 4-input NOR | 100 | 1 | 100 |
| | | | 250 |

Table 2.1: Propagation delay for the 4x6 decoder of the arithmetic functional block

| Gate Type | Propagation Delay (ps) | Number of Gates in Critical Path | Total Propagation Delay (ps) |
|-------------|------------------------|----------------------------------|------------------------------|
| inverter | 25 | 1 | 25 |
| 4-input AND | 125 | 1 | 125 |
| 5 x 1 mux | 175 | 1 | 175 |
| | | | 325 |

Table 2.2: Propagation delay for an opcode bit to the output for the logical functional block

| Functional Block Type | Propagation Delay (ps) | Number of FBs in Critical Path | Total Propagation Delay (ps) |
|-----------------------|------------------------|--------------------------------|------------------------------|
| 4 x 6 Decoder | 250 | 1 | 250 |
| 3 x 1 Mux | 225 | 1 | 225 |
| Ripple Carry Adder | 1075 | 1 | 1075 |
| | | | 1550 |

Table 2.3: Propagation delay for the arithmetic functional block

| Gate Type | Propagation Delay (ps) | Number of Gates in Critical Path | Total Propagation Delay (ps) |
|--------------|------------------------|----------------------------------|------------------------------|
| 2-input NAND | 50 | 1 | 50 |
| 3-input NAND | 75 | 1 | 75 |
| | | | 125 |

Table 2.4: Propagation delay for the 3 x 1 mux used for the function unit

| Functional Block Type | Propagation Delay (ps) | Number of FBs in Critical Path | Total Propagation Delay (ps) |
|-----------------------|------------------------|--------------------------------|------------------------------|
| Arithmetic FB | 1550 | 1 | 1550 |
| 3 x 1 Mux | 125 | 1 | 125 |
| | | | 1675 |

Table 2.5: Propagation delay for the function unit

| Gate Type | Propagation Delay (ps) | Number of Gates in Critical Path | Total Propagation Delay (ps) |
|--------------|------------------------|----------------------------------|------------------------------|
| inverter | 25 | 1 | 25 |
| 3-input NAND | 75 | 1 | 75 |
| | | | 100 |

Table 2.6: Propagation delay for the 2x4 load decoder of the register transfer system

| Gate Type | Propagation Delay (ps) | Number of Gates in Critical Path | Total Propagation Delay (ps) |
|--------------|------------------------|----------------------------------|------------------------------|
| inverter | 25 | 1 | 25 |
| 2-input NAND | 50 | 1 | 50 |
| | | | 75 |

Table 2.7: Propagation delay for the mux decoder of the register transfer system

| Block / Gate Type | Propagation Delay (ps) | Number of Gates/Blocks in Critical Path | Total Propagation Delay (ps) |
|-------------------|------------------------|---|------------------------------|
| 2x4 Decoder | 75 | 1 | 75 |
| 2-input NAND | 50 | 1 | 50 |
| 4-input NAND | 100 | 1 | 100 |
| | | | 225 |

Table 2.8: Propagation delay for the 4x1 mux of the register transfer system

| Block Type | Propagation Delay (ps) | Number of Blocks in Critical Path | Total Propagation Delay (ps) |
|------------------|------------------------|-----------------------------------|------------------------------|
| 2x4 Load Decoder | 100 | 1 | 100 |
| 4x1 Mux | 225 | 1 | 225 |
| | | | 325 |

Table 2.9: Propagation delay for the register transfer system

| Circuit Type | Propagation Delay (ps) | Number of Circuits in Critical Path | Total Propagation Delay (ps) |
|--------------------------|------------------------|-------------------------------------|------------------------------|
| Function Unit | 1675 | 1 | 1675 |
| Register Transfer System | 325 | 1 | 325 |
| | | | 2000 |

Table 2.10: Propagation delay for the entire circuit (2x4 decoder input → function unit output)

Simulation Results

This circuit was simulated using the Quartus Prime Lite Edition software. The results from the simulation and testing can be found in Diagram 2. The simulation loads each register by setting KEY[0] to low, indicated by the text LOAD or LD, then proceeds to execute each operation the function unit is capable of and store it in one of the registers, indicated by setting KEY[1] to low. Note that two non-adjacent columns of the waveform having the same color does not indicate any special relation between them, as colors had to be reused due to the significant number of columns.

 


Diagram 2: The annotated waveform with the inputs and corresponding operations

Conclusion

Project LE C required the design of a function unit and a register transfer system that were combined to execute and store the results of various operations. The assignment required that the function unit could implement 13 distinct operations, the function unit had to accept two 8-bit operands and output an 8-bit result along with four status bits, the register transfer system had four registers that each stored 8 bits, any two of the registers could send their data to the function unit, and any of the registers could receive either the output of the function unit or data from the switches. The assignment also required that the circuit was verified through a

simulation in the Quartus Prime Lite Edition software. The circuit was then implemented on the DE10-Lite Board to test it physically, and was found to function as expected.